

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A Date: 01/09/2024
------------------	-----------------------	-----------------------------------


Week# 3 Program Number: 1

TITLE:


WRITE A VERILOG PROGRAM TO MODEL A HALF ADDER THAT CAN ADD TWO BITS. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

 

Schematic

 

Realization

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

```
fulladd_tb.v x fulladd.v
Users > abhishekp > Downloads > verilog > fulladd_tb.v
1  module halfadd_tb;
2  reg aa, bb;
3  wire ss,cy;
4  halfadd add1(.a(aa),.b(bb),.sum(ss),.cout(cy));
5  initial
6  begin
7  $dumpfile("halfadd_test.vcd");
8  $dumpvars(0, halfadd_tb);
9  end
10 initial
11 begin
12 $monitor($time, "A=%b, B=%b, SUM=%b, CARRY=%b", aa, bb,ss, cy);
13 aa=1'b0; bb=1'b0;
14 #5
15 aa=1'b0; bb=1'b1;
16 #5
17 aa=1'b1; bb=1'b0;
18 #5
19 aa=1'b1; bb=1'b1;
20 end
21 endmodule
```

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

≡ fulladd_tb.v

≡ fulladd.v ×


Users > abhishekp > Downloads > verilog > ≡ fulladd.v

```
1  module and2( a, b, cout);
2  input a,b;
3  output cout;
4  assign cout=a&b;
5  endmodule
6  module xor2( a, b,sum);
7  input a,b;
8  output sum;
9  assign sum=a^b;
10 endmodule
11 module halfadd(a,b, sum, cout);
12 input a,b;
13 output sum;
14 output cout;
15 xor2 x (a,b,sum);
16 and2 a0(a,b,cout);
17 endmodule
```

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

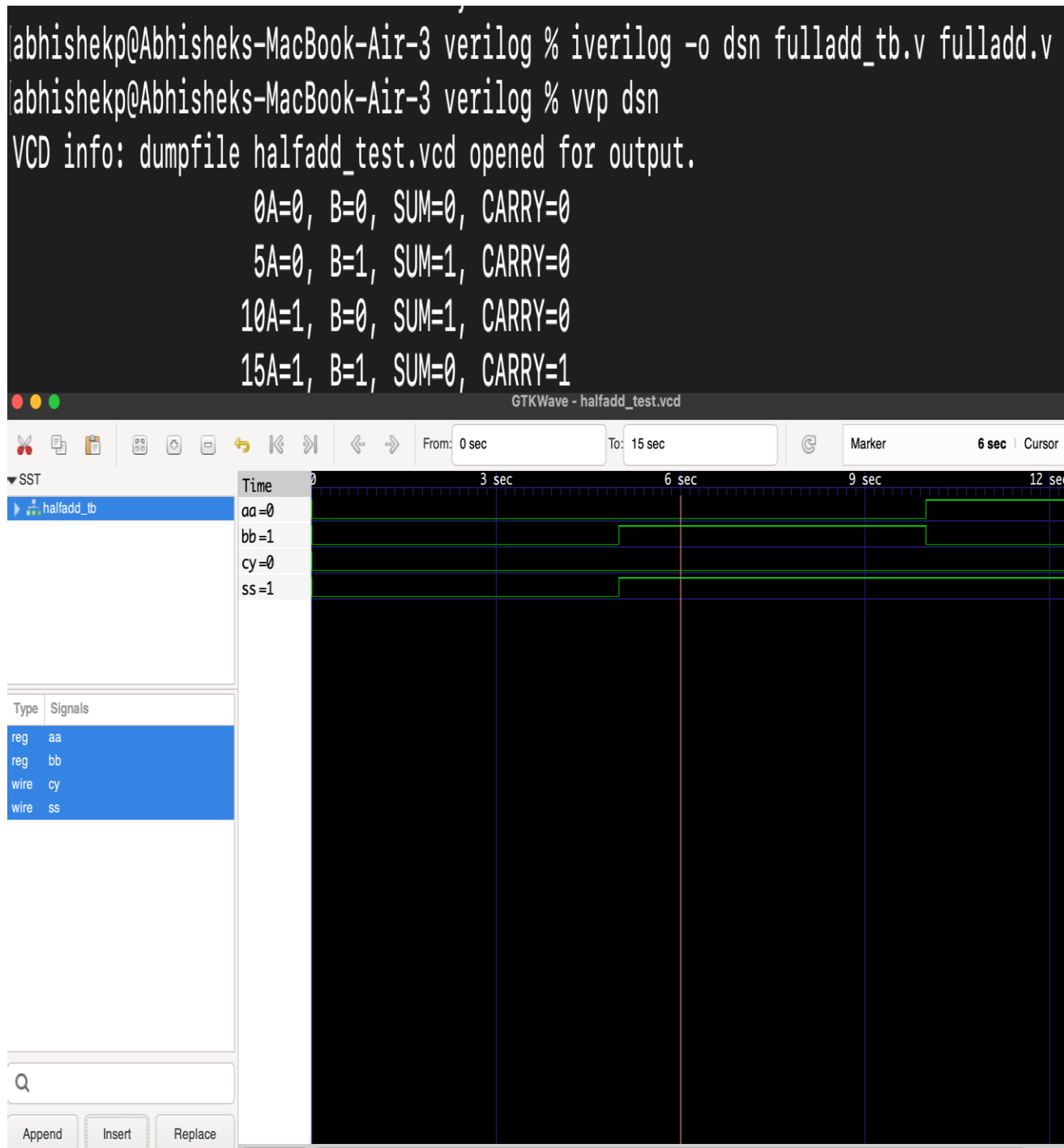

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A Date: 01/09/2024
------------------	-----------------------	-----------------------------------

Week#____3_____

Program Number: ____2____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A FULL ADDER THAT CAN ADD TWO BITS ALONG WITH AN INPUT CARRY. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

```
fulladd.v
1  module fulladd(input wire a, b, cin, output wire sum, cout);
2  wire [4:0] t;
3
4      xor2 x0(a, b, t[0]);
5      xor2 x1(t[0], cin, sum);
6
7      and2 a0(a, b, t[1]);
8      and2 a1(a, cin, t[2]);
9      and2 a2(b, cin, t[3]);
10
11     or2 o0(t[1], t[2], t[4]);
12     or2 o1(t[3], t[4], cout);
13 endmodule
14
```

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

```
1  module fulladd_tb;
2
3  reg aa,bb,cc;
4
5  wire ss,cy;
6
7  fulladd add1(.a(aa), .b(bb), .cin(cc), .sum(ss), .cout(cy));
8
9  initial
10
11  begin
12
13  $dumpfile("fulladd_test.vcd");
14
15  $dumpvars(0, fulladd_tb);
16
17  end
18  |
19
20  initial
21  |
22  | begin
23  | $monitor($time, "a=%b, b=%b, c=%b,sum=%b,carry=%b", aa,bb,cc,ss,cy);
24  | aa = 1'b0;
25  | bb = 1'b0;
26  | cc=1'b0;
27  |
28  | #5
29  | | aa = 1'b0;
30  | | bb = 1'b0;
31  | | cc=1'b1;
32  | |
33  | | #5
34  | | | aa = 1'b0;
35  | | | bb = 1'b1;
36  | | | cc=1'b0;
37  | | |
38  | | | #5
39  | | | | aa = 1'b0;
40  | | | | bb = 1'b1;
41  | | | | cc=1'b1;
42  | | | |
43  | | | | #5
44  | | | | | aa = 1'b1;
45  | | | | | bb = 1'b0;
46  | | | | | cc=1'b0;
47  | | | | |
48  | | | | | #5
49  | | | | | | aa = 1'b1;
50  | | | | | | bb = 1'b0;
51  | | | | | | cc=1'b1;
52  | | | | | |
53  | | | | | | #5
54  | | | | | | | aa = 1'b1;
55  | | | | | | | bb = 1'b1;
56  | | | | | | | cc=1'b0;
57  | | | | | | |
58  | | | | | | | #5
59  | | | | | | | | aa = 1'b0;
60  | | | | | | | | bb = 1'b1;
61  | | | | | | | | cc=1'b1;
62  | | | | | | | |
63  | | | | | | | | end
64  | endmodule
65
66
67
```


Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

```
abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn
VCD info: dumpfile fulladd_test.vcd opened for output.
```
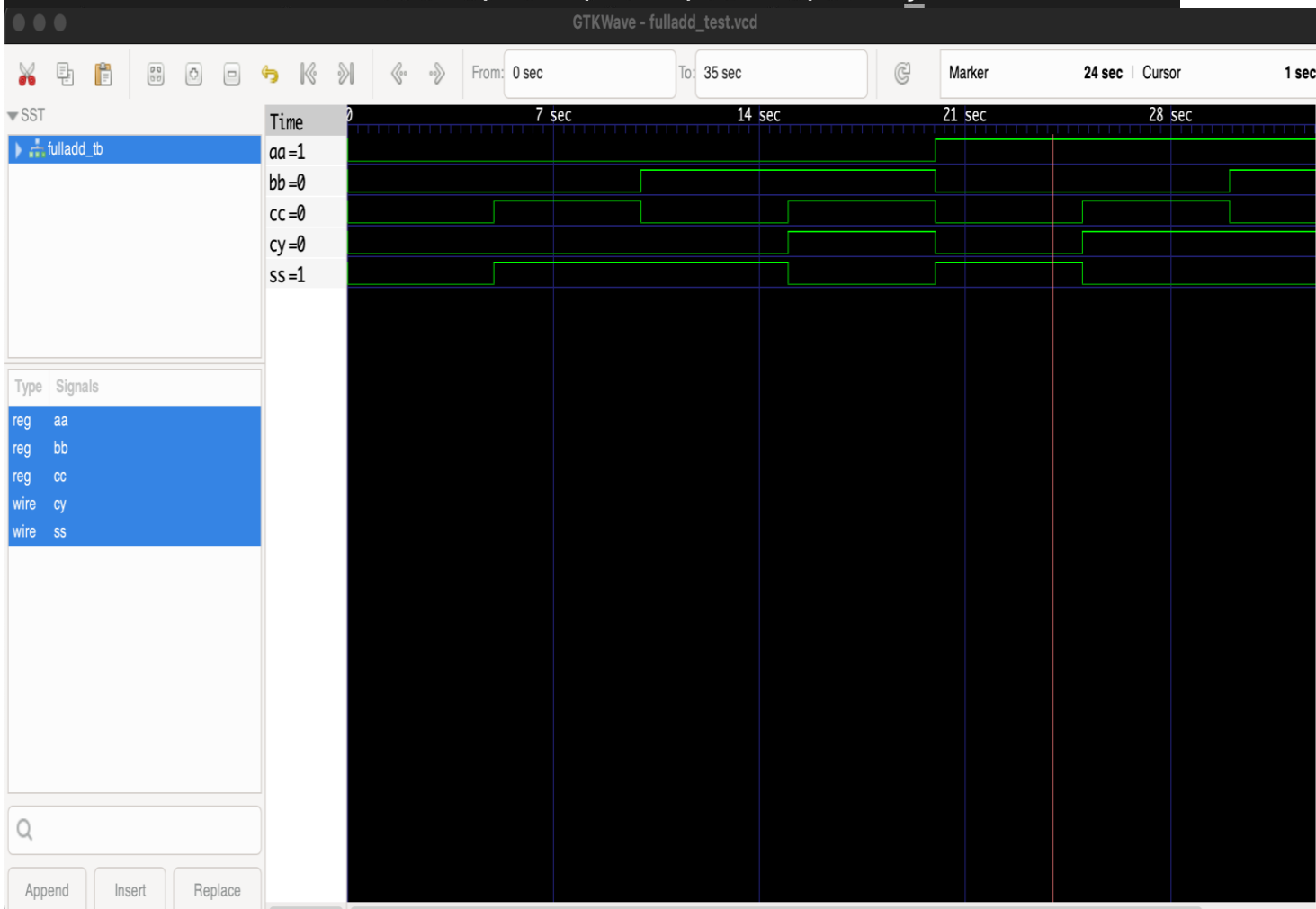
```
0a=0, b=0, c=0, sum=0, carry=0
5a=0, b=0, c=1, sum=1, carry=0
10a=0, b=1, c=0, sum=1, carry=0
15a=0, b=1, c=1, sum=0, carry=1
20a=1, b=0, c=0, sum=1, carry=0
25a=1, b=0, c=1, sum=0, carry=1
30a=1, b=1, c=0, sum=0, carry=1
35a=0, b=1, c=1, sum=0, carry=1
```



Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	-----------------------	------------

Week# ____1____

Program Number: ____3____

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A FOUR BIT FULL ADDER THAT GENERATES A FOUR BIT SUM AND A 1 BIT CARRY OUTPUT. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

```
1 // Module 4-bit ripple carry adder.
2
3 module fulladdR(input wire [3:0] a, b, input wire cin, output wire [3:0] sum, output wire cout);
4
5     // Instantiate full adder modules here.
6     wire [2:0] c;
7     fulladd u0 (a[0], b[0], cin, sum[0], c[0]);
8     fulladd u1 (a[1], b[1], c[0], sum[1], c[1]);
9     fulladd u2 (a[2], b[2], c[1], sum[2], c[2]);
10    fulladd u3 (a[3], b[3], c[2], sum[3], cout);
11
12 endmodule
13
14
```


Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24


```
1  `timescale 1 ns / 100 ps
2
3  `define TESTVECS 10
4  module tb;
5
6  reg clk, reset;
7
8  reg [3:0] i0, i1;
9  reg cin;
10
11 wire [3:0] o;
12 wire cout;
13
14 reg [8:0] test_vecs [0:(`TESTVECS-1)];
15
16 integer i;
17
18 initial
19 begin
20 $dumpfile("rca_test.vcd");
21
22 $dumpvars(0,tb);
23
24 end
25
26 initial
27 begin
28 reset = 1'b1; #12.5 reset = 1'b0; end
29 initial clk = 1'b0; always #5 clk =~ clk;
30
31 initial begin
32
33 test_vecs[0] = 9'b000000000;
34
35 test_vecs[1] = 9'b000000001;
36
37 test_vecs[2] = 9'b000100010;
38
39 test_vecs[3] = 9'b000100011;
40
41 test_vecs[4] = 9'b001000100;
42
43 test_vecs[5] = 9'b101010110;
44
45 test_vecs[6] = 9'b101010111;
46
47 test_vecs[7] = 9'b110011010;
48
49 test_vecs[8] = 9'b111111100;
50
51 test_vecs[9] = 9'b111111101;
52
53
54 end
55 initial {i0, i1, cin, i} = 0;
56 fulladdR u0 (i0, i1, cin, o, cout);
57 initial begin
58 #6 for(i=0;i<`TESTVECS;i=i+1)
59 begin #10 {i0, i1, cin}=test_vecs[i]; end
60 #100 $finish;
61 end
62
63 always@(i0 or i1 or cin)
64 $monitor("At time = %t, i0=%b, i1=%b,cin=%b,Sum = %b,Carry %b", $time,i0,i1,cin,o,cout);
65
66
67 endmodule
68
```

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24


```
Last login: Wed Oct 2 19:07:14 on ttys000
abhishekp@Abhisheks-MacBook-Air-3 ~ % cd downloads
abhishekp@Abhisheks-MacBook-Air-3 downloads % iverilog -o dsn basicfa.v rca_tb.v rca.v
abhishekp@Abhisheks-MacBook-Air-3 downloads % vvp dsn
VCD info: dumpfile rca_test.vcd opened for output.
At time = 0, i0=0000, i1=0000,cin=0,Sum = 0000,Carry 0
At time = 260, i0=0000, i1=0000,cin=1,Sum = 0001,Carry 0
At time = 360, i0=0001, i1=0001,cin=0,Sum = 0010,Carry 0
At time = 460, i0=0001, i1=0001,cin=1,Sum = 0011,Carry 0
At time = 560, i0=0010, i1=0010,cin=0,Sum = 0100,Carry 0
At time = 660, i0=1010, i1=1011,cin=0,Sum = 0101,Carry 1
At time = 760, i0=1010, i1=1011,cin=1,Sum = 0110,Carry 1
At time = 860, i0=1100, i1=1101,cin=0,Sum = 1001,Carry 1
At time = 960, i0=1111, i1=1110,cin=0,Sum = 1101,Carry 1
At time = 1060, i0=1111, i1=1110,cin=1,Sum = 1110,Carry 1
rca_tb.v:60: $finish called at 2060 (100ps)
abhishekp@Abhisheks-MacBook-Air-3 downloads % gtkwave rca_test.vcd
```

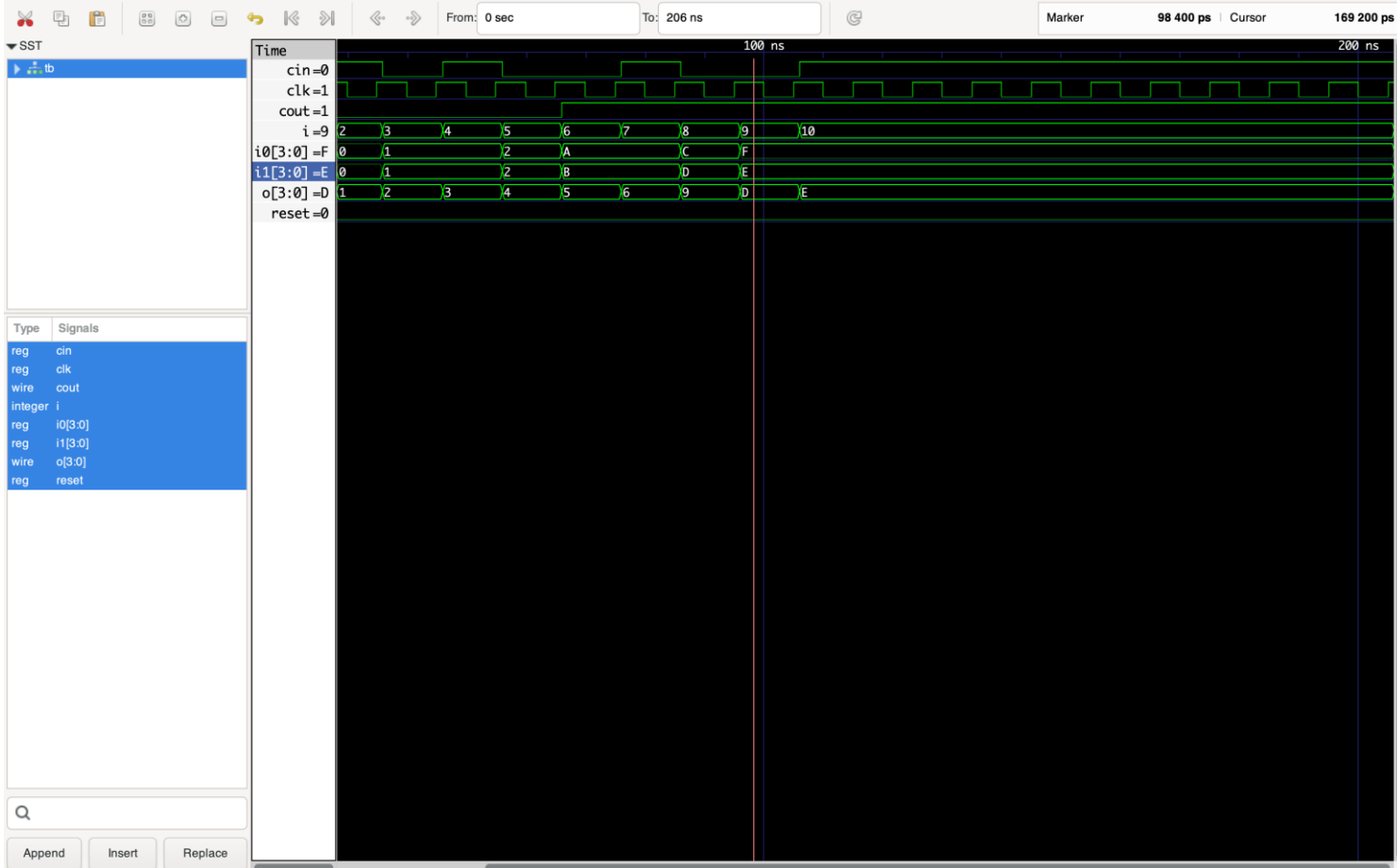

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature:

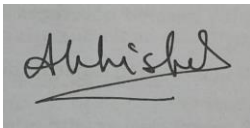A handwritten signature in black ink, appearing to read 'Abhishek', with a horizontal line underneath.

Name:

ABHISHEK P

SRN:

PES2UG23AM002

Section: A