

# Digital Design and Computer Organisation Laboratory

## 3rd Semester, Academic Year 2024

DATE : 11/8/2024

NAME: ABHISHEKP

SRN : PES2UG23AM002

SECTION:A

### WEEK1

### PROGRAM-1

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT AND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

### ANDGATE


```
module andgate(  
    input a,  
    input b,  
    output y  
);  
assign y = a&b;  
endmodule
```

```
module and_test;  
    reg a, b;  
    wire y;  
    and and_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("and_gate.vcd");  
        $dumpvars(0, and_test);  
    end  
endmodule
```

### ANDGATE VVP OUTPUT SCREENSHOT

```
VCD info: dumpfile and_gate.vcd opened for output.  
0 a = 0, b = 0, y = 0  
10 a = 0, b = 1, y = 0  
20 a = 1, b = 0, y = 0  
30 a = 1, b = 1, y = 1
```

### ANDGATEGTKWAVE:

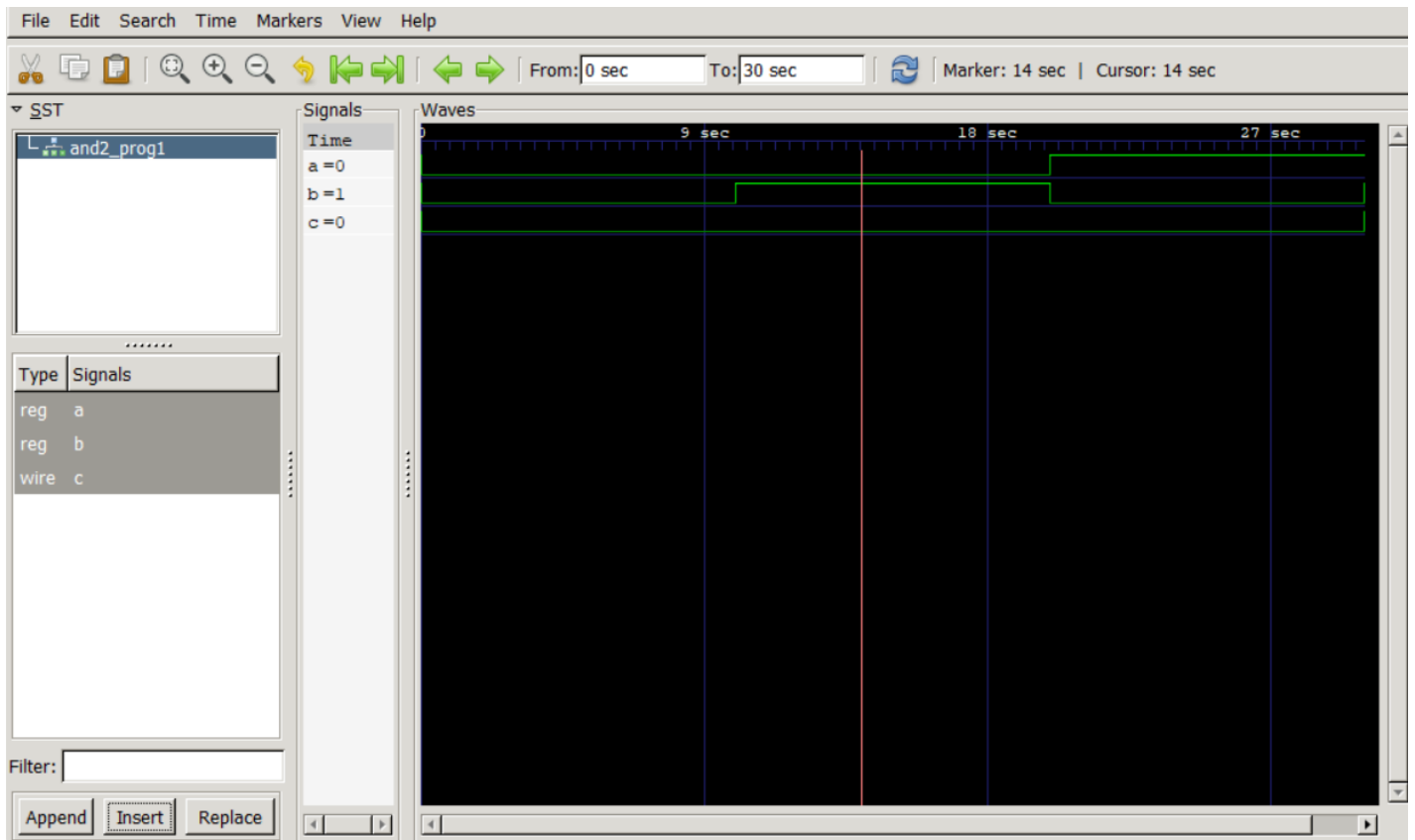

### ANDGATETRUTHTABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

## PROGRAM: 2

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT OR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTK WAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE OR GATE TRUTH TABLE

### ORGATE CODE


```
module orgate(  
    input a,  
    input b,  
    output y  
);  
assign y = a|b;  
endmodule
```

```
module or_test;  
    reg a, b;  
    wire y;  
    or or_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("or_gate.vcd");  
        $dumpvars(0, or_test);  
    end  
endmodule
```

### ORGATE VVP OUTPUT

```
VCD info: dumpfile or_gate.vcd opened for output.  
0 a = 0, b = 0, y = 0  
10 a = 0, b = 1, y = 1  
20 a = 1, b = 0, y = 1  
30 a = 1, b = 1, y = 1  
[Done] exit with code=0 in 0.275 seconds
```

### ORGATEGTKWAVEOUTPUT:

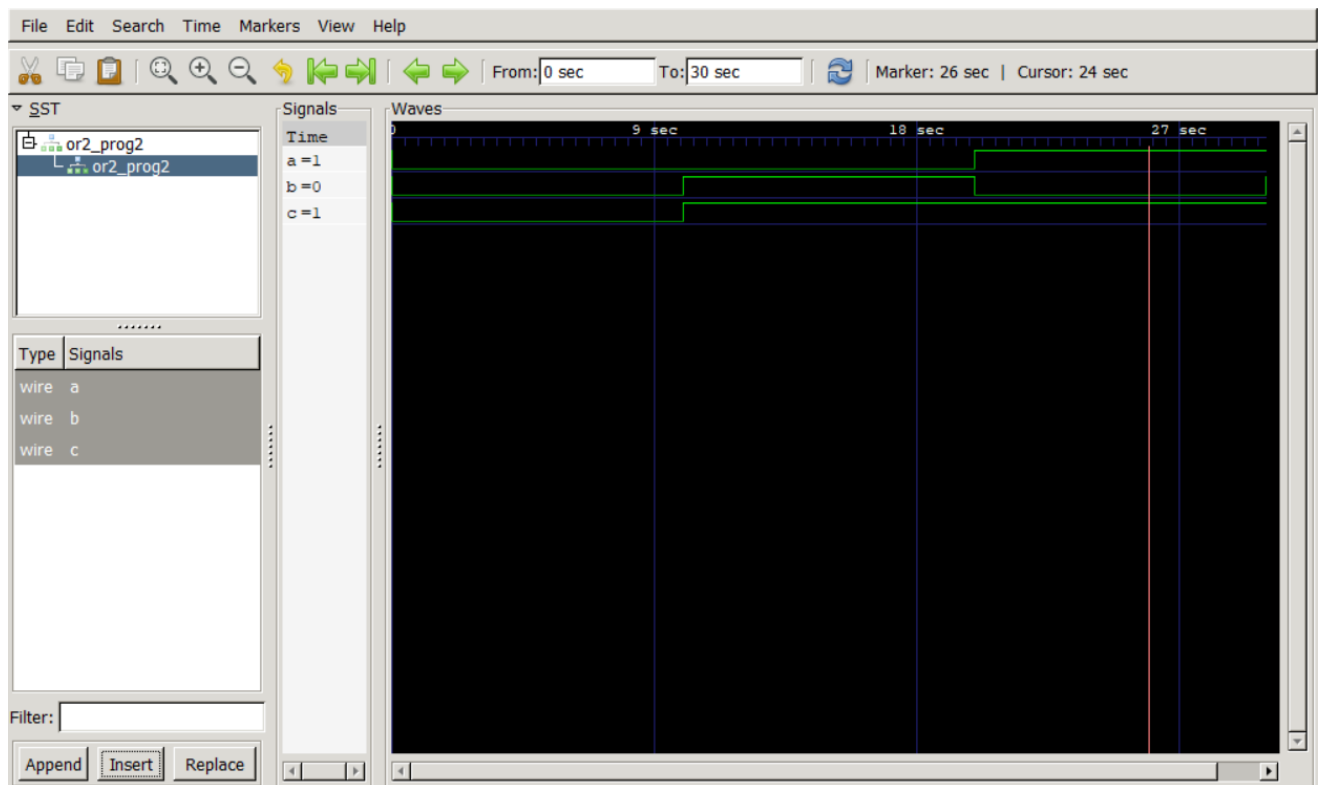

### ORGATETRUTHTABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

WRITE A VERILOG PROGRAM TO MODEL A NOT GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOT GATE TRUTH TABLE

NOT GATE CODE:


```
module notgate(  
    input a,  
    output y);  
    assign y=~a;  
endmodule
```

```
module not_test;  
    reg a;  
    wire y;  
    not not_test(y,a);  
    initial begin  
        #0 a=0;  
        #10 a=1;  
    end  
    initial begin  
        $monitor($time, " a = %b, y = %b", a, y);  
    end  
    initial begin  
        $dumpfile("not_gate.vcd");  
        $dumpvars(0, not_test);  
    end  
endmodule
```

NOT GATE VVP OUTPUT:

```
VCD info: dumpfile not_gate.vcd opened for output.  
0 a = 0, y = 1  
10 a = 1, y = 0  
[Done] exit with code=0 in 0.425 seconds
```

NOT GATE GTKWAVE:

 

### NOTGATETRUTHTABLE:

INPUT	OUTPUT
A	Y
0	1
1	0

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NAND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NAND GATE TRUTH TABLE

NAND GATE CODE:


```
module nandgate(  
    input a,  
    input b,  
    output y  
);  
assign y = ~(a&b);  
endmodule
```

```
module nand_test;  
    reg a, b;  
    wire y;  
    nand nand_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("nand_gate.vcd");  
        $dumpvars(0, nand_test);  
    end  
endmodule
```

NAND GATE VVP OUTPUT:

```
VCD info: dumpfile nand_gate.vcd opened for output.  
0 a = 0, b = 0, y = 1  
10 a = 0, b = 1, y = 1  
20 a = 1, b = 0, y = 1  
30 a = 1, b = 1, y = 0  
[Done] exit with code=0 in 0.263 seconds
```

NAND GATE GTKWAVE OUTPUT:

 

NANDGATETRUTHTABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOR GATE TRUTH TABLE

NOR GATE CODE:


```
module norgate(  
    input a,  
    input b,  
    output y  
);  
assign y = ~(a|b);  
endmodule
```

```
module nor_test;  
    reg a, b;  
    wire y;  
    nor nor_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("nor_gate.vcd");  
        $dumpvars(0, nor_test);  
    end  
endmodule
```

NOR GATE VVP OUTPUT:

```
VCD info: dumpfile nor_gate.vcd opened for output.  
0 a = 0, b = 0, y = 1  
10 a = 0, b = 1, y = 0  
20 a = 1, b = 0, y = 0  
30 a = 1, b = 1, y = 0  
[Done] exit with code=0 in 0.284 seconds
```

NOR GATE GTKWAVE OUTPUT:

 

### NORGATETRUTHTABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

XOR GATE CODE:


```
module Xorgate(  
    input a,  
    input b,  
    output y  
);  
    assign y = a^b;  
endmodule
```

```
module xor_test;  
    reg a, b;  
    wire y;  
    xor xor_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("xor_gate.vcd");  
        $dumpvars(0, xor_test);  
    end  
endmodule
```

XOR GATE VVP OUTPUT:

```
VCD info: dumpfile xor_gate.vcd opened for output.  
0 a = 0, b = 0, y = 0  
10 a = 0, b = 1, y = 1  
20 a = 1, b = 0, y = 1  
30 a = 1, b = 1, y = 0  
[Done] exit with code=0 in 0.196 seconds
```

XOR GATE GTKWAVE OUTPUT:

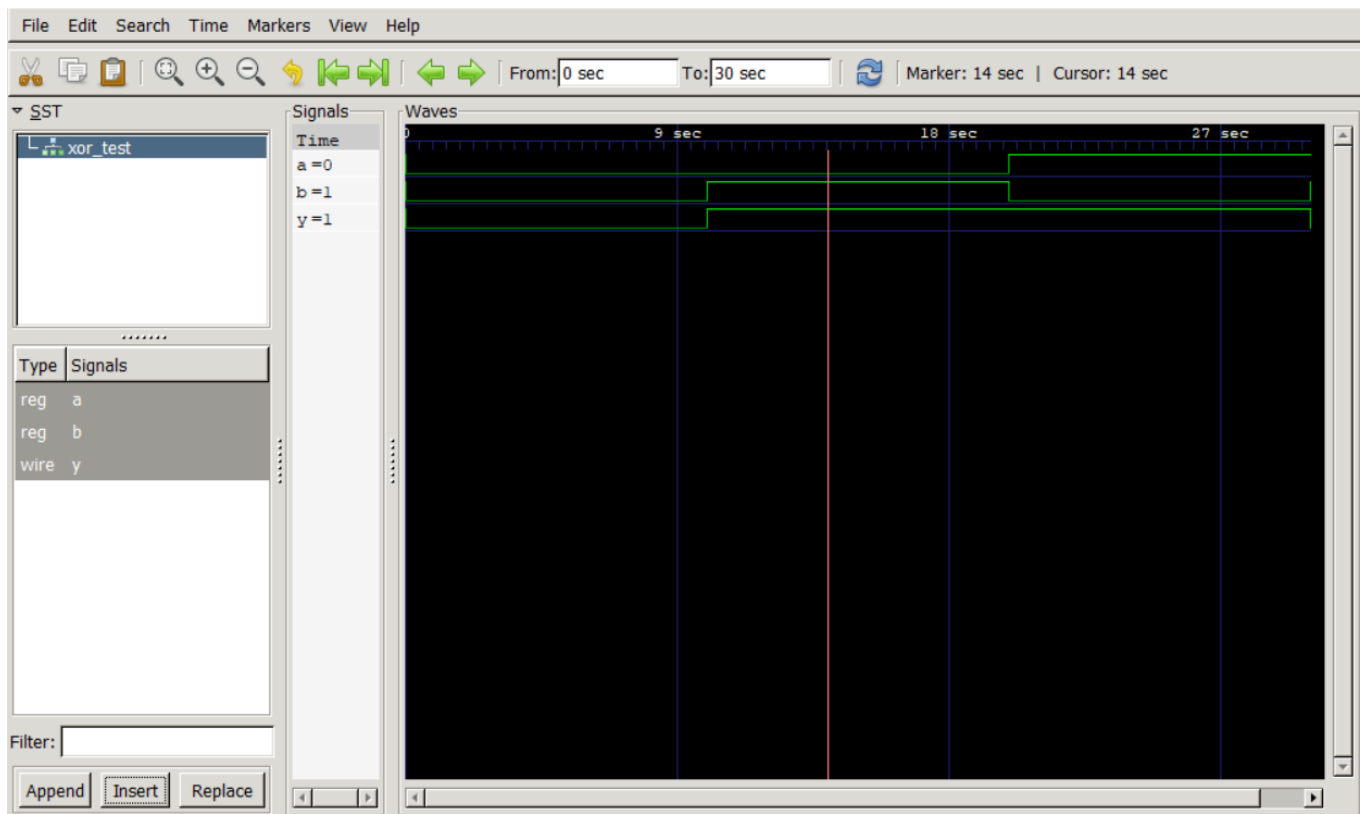

#### XORGATE TRUTH TABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XNOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

XNOR GATE CODE:


```
module xnorgate(  
    input a,  
    input b,  
    output y  
);  
    assign y = ~(a^b);  
endmodule
```

```
module xnor_test;  
    reg a, b;  
    wire y;  
    xnor xnor_test (y, a, b);  
    initial begin  
        #0 a = 0; b = 0;  
        #10 a = 0; b = 1;  
        #10 a = 1; b = 0;  
        #10 a = 1; b = 1;  
    end  
    initial begin  
        $monitor($time, " a = %b, b = %b, y = %b", a, b, y);  
    end  
    initial begin  
        $dumpfile("xnor_gate.vcd");  
        $dumpvars(0, xnor_test);  
    end  
endmodule
```

XNOR GATE VVP OUTPUT:

```
VCD info: dumpfile xnor_gate.vcd opened for output.  
0 a = 0, b = 0, y = 1  
10 a = 0, b = 1, y = 0  
20 a = 1, b = 0, y = 0  
30 a = 1, b = 1, y = 1  
[Done] exit with code=0 in 0.218 seconds
```

XNOR GATE GTKWAVE OUTPUT:

 

### XNOR GATE TRUTH TABLE:

INPUTS		OUTPUTS
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

NAME : ABHISHEK P

---

---

SRN :

PES2UG23AM002

SECTION : A