

# Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Date: 09/09/2024


Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------

Week# 4

Program Number: 1

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A 2: 1 MULTIPLEXER. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

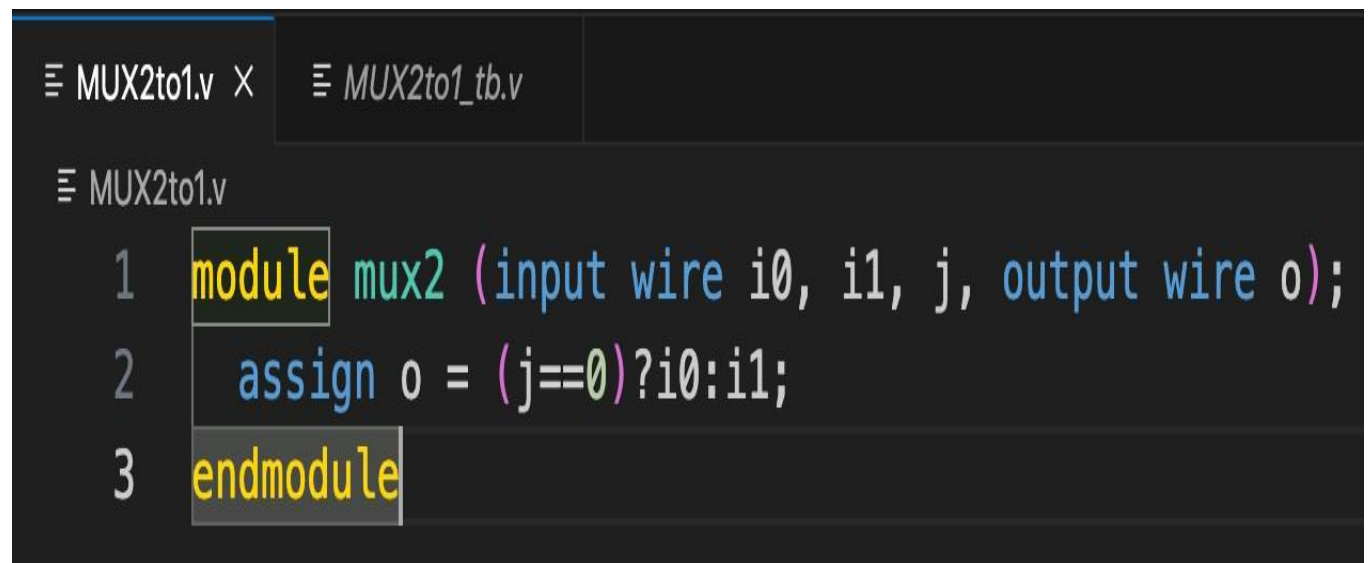A screenshot of a Verilog code editor. The top bar shows two tabs: 'MUX2to1.v' and 'MUX2to1\_tb.v'. The main editor area shows the code for 'MUX2to1.v'. The code is as follows:

```
1 module mux2 (input wire i0, i1, j, output wire o);  
2     assign o = (j==0)?i0:i1;  
3 endmodule
```

≡ MUX2to1.v

≡ MUX2to1\_tb.v ×


≡ MUX2to1\_tb.v

```
1  module TB;
2  reg A,B,S;
3  wire X;
4  initial
5  begin
6  $dumpfile("MUX2_test.vcd");
7  $dumpvars(0,TB);
8  end
9  mux2 newMUX(.i0(A), .i1(B), .j(S), .o(X));
10 initial
11 begin
12 #5 S = 1'b0;
13 A = 1'b0;
14 B = 1'b0;
15 #5 S = 1'b0;A = 1'b0;
16 B = 1'b1;
17 #5
18 S = 1'b0;A = 1'b1;
19 B = 1'b0;
20 #5
21 S = 1'b0;A = 1'b1;
22 B = 1'b1;
23 #5
24 | S = 1'b1;
25 A = 1'b0;
26 B = 1'b0;
27 #5
28 | S = 1'b1;A = 1'b0;
29 B = 1'b1;
30 #5
31 | S = 1'b1;A = 1'b1;
32 B = 1'b0;
33 #5
34 | S=1'b1;A = 1'b1;
35 B = 1'b1;
36 #5;
37 end
38 always@(A or B or S)
39 $monitor("At time = %t,S=%b, A=%b, B=%b,Output = %b",$time,S,A,B, X);
40 endmodule
```

```

abhishekp@Abhisheks-MacBook-Air-3 ~ % cd Downloads
abhishekp@Abhisheks-MacBook-Air-3 Downloads % cd verilog
abhishekp@Abhisheks-MacBook-Air-3 verilog % iverilog -o dsn MUX2to1_tb.v MUX2to1.v
abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn
VCD info: dumpfile MUX2_test.vcd opened for output.
At time =          5,S=0, A=0, B=0,Output = 0
At time =         10,S=0, A=0, B=1,Output = 0
At time =         15,S=0, A=1, B=0,Output = 1
At time =         20,S=0, A=1, B=1,Output = 1
At time =         25,S=1, A=0, B=0,Output = 0
At time =         30,S=1, A=0, B=1,Output = 1
At time =         35,S=1, A=1, B=0,Output = 0
At time =         40,S=1, A=1, B=1,Output = 1
abhishekp@Abhisheks-MacBook-Air-3 verilog % gtkwave MUX2_test.vcd

```

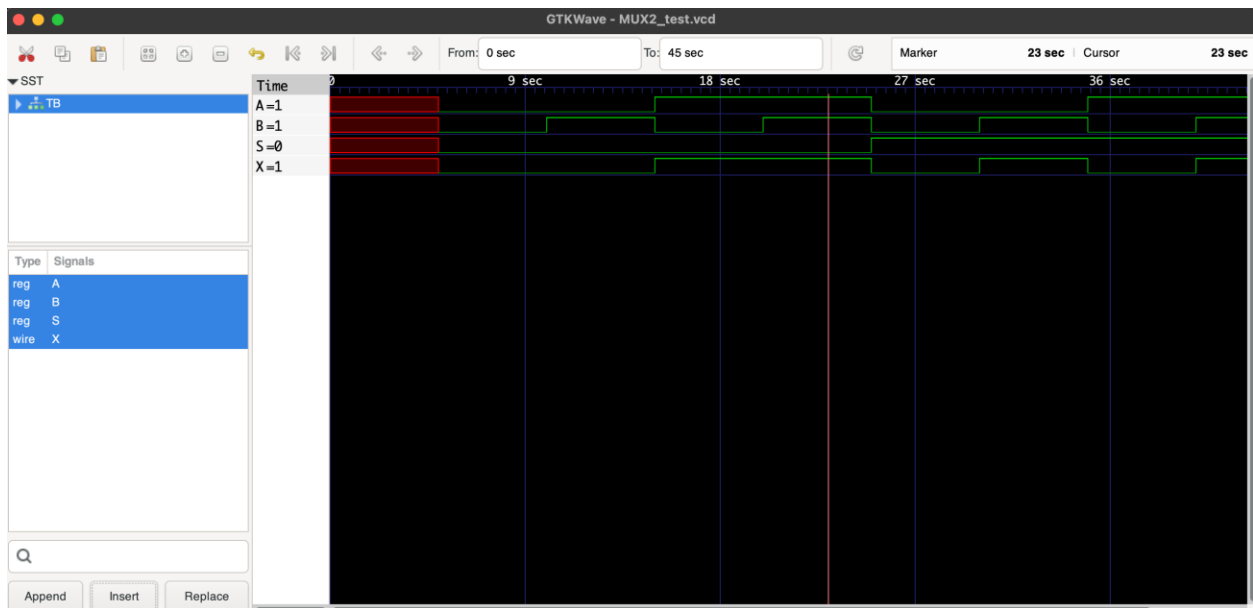

**Digital Design and Computer Organisation Laboratory**

**UE22CS251A**

**3rd Semester, Academic Year 2023-24**

**Date: 09/09/2024**

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	-----------------------	------------

Week#\_\_\_\_4\_\_\_\_\_

Program Number:\_\_\_\_2\_\_\_\_\_

TITLE :

**WRITE A VERILOG PROGRAM TO MODEL A 4:1 MULTIPLEXER USING 2:1 MULTIPLEXERS. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**


≡ MUX4to1.v

```
1  module mux4 (input wire [0:3] i, input wire j1, j0, output wire o);
2      wire t0, t1;
3      mux2 mux2_0 (i[0], i[1], j1, t0);
4      mux2 mux2_1 (i[2], i[3], j1, t1);
5      mux2 mux2_2 (t0, t1, j0, o);
6  endmodule
```

tb\_MUX4to1.v

```
1 module TB;
2 reg [0:3] ii;
3 reg s0;
4 reg s1;
5 wire yy;
6 initial
7 begin
8 $dumpfile("MUX4_test.vcd");
9 $dumpvars(0, TB);
10 end
11 mux4 newMUX(.i(ii), .j0(s0), .j1(s1), .o(yy));
12 initial
13 begin
14 #5
15     ii = 4'b1000;
16     s0=1'b0;
17     s1=1'b0;
18     #5
19     ii= 4'b0100;
20     s0=1'b0;
21     s1=1'b1;
22     #5
23     ii = 4'b0010;
24     s0=1'b1;
25     s1=1'b0;
26     #5
27     ii = 4'b0001;
28     s0=1'b1;
29     s1=1'b1;
30     #5;
31 end
32 always@(ii or s0 or s1)
33 $monitor("At time = %t,Inputs=%b, s0=%b, s1=%b,Output = %b", $time, ii, s0, s1, yy);
34 endmodule
```

```
abhishekp@Abhisheks-MacBook-Air-3 verilog % iverilog -o dsn MUX2to1.v MUX4to1.v tb_MUX4to1.v
abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn
VCD info: dumpfile MUX4_test.vcd opened for output.
At time = 5,Inputs=1000, s0=0, s1=0,Output = 1
At time = 10,Inputs=0100, s0=0, s1=1,Output = 1
At time = 15,Inputs=0010, s0=1, s1=0,Output = 1
At time = 20,Inputs=0001, s0=1, s1=1,Output = 1
abhishekp@Abhisheks-MacBook-Air-3 verilog % gtkwave MUX4_test.vcd
```

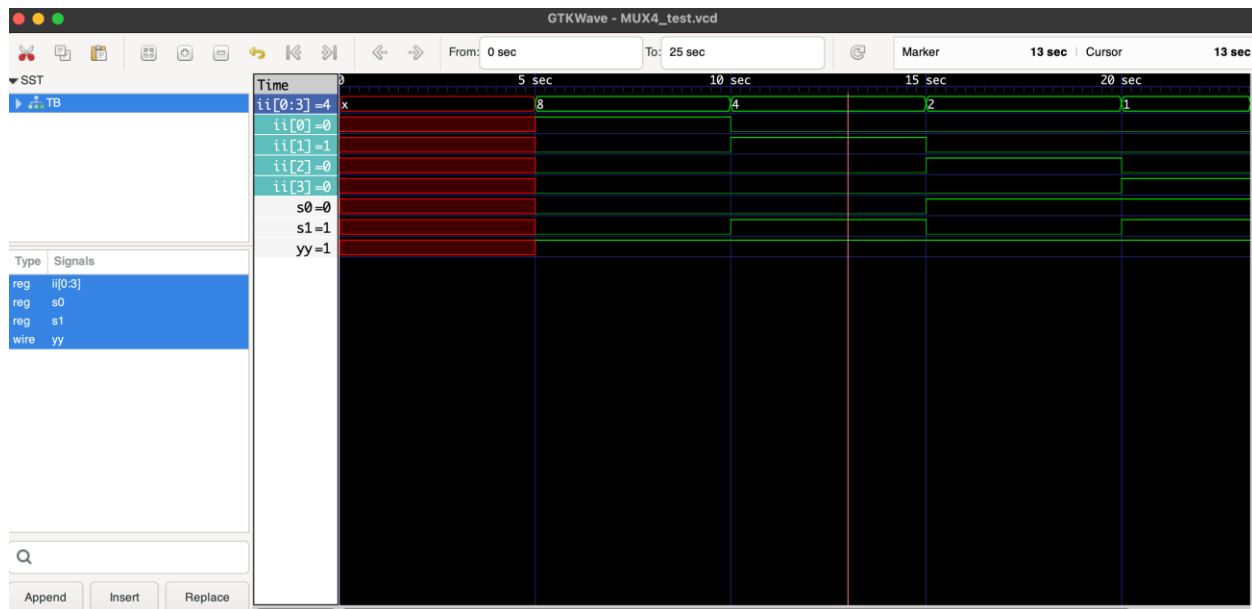

**Digital Design and Computer Organisation Laboratory**

**UE22CS251A**

**3rd Semester, Academic Year 2023-24**

**Date: 09/09/2024**

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------

Week# 4

Program Number: 3

**TITLE:**

**WRITE A VERILOG PROGRAM TO MODEL A 1:2 DEMULTIPLEXER. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**

≡ MUX2to1.v ×

≡ MUX2to1\_tb.v

≡ MUX2to1.v

```
1  module demux_1_to_2 (  
2    input wire D,  
3    input wire S,  
4    output wire Y0,  
5    output wire Y1  
6  );  
7    assign Y0 = (S == 0)? D:0;  
8    assign Y1 = (S == 1)? D:0;  
9  endmodule
```


≡ MUX2to1.v

≡ MUX2to1\_tb.v ×

≡ MUX2to1\_tb.v

```
1  module tb_demux_1_to_2;
2  reg D;
3  reg S;
4  wire Y0;
5  wire Y1;
6  demux_1_to_2 uut (
7  .D(D),
8  .S(S),
9  .Y0(Y0),
10 .Y1(Y1)
11 );
12 initial begin
13 D = 0; S = 0;
14 #10;
15 D = 0; S = 0;
16 #10;
17 D= 1; S = 0;
18 #10;
19 D = 0; S = 1;
20 #10;
21 D= 1; S = 1;
22 #10;
23 $finish;
24 end
25 initial begin
26 $monitor("Time=%0t D=%b S=%b Y0=%b Y1=%b", $time, D, S, Y0, Y1);
27 end
28 initial begin
29 $dumpfile("demux.vcd");
30 $dumpvars(0, tb_demux_1_to_2);
31 end
32 endmodule
```



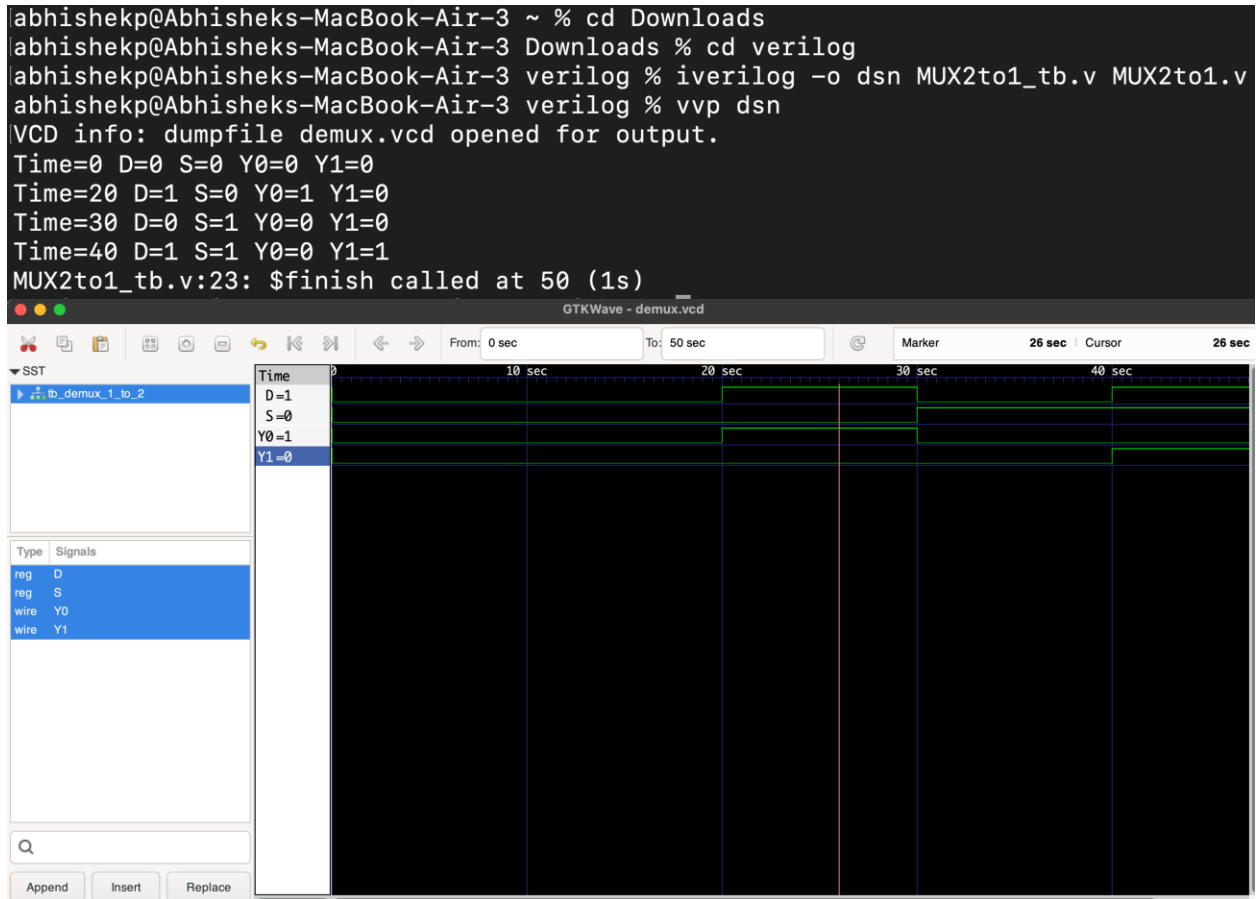

**Digital Design and Computer Organisation Laboratory**

**UE22CS251A**

**3rd Semester, Academic Year 2023-24**

**Date: 09/09/2024**


Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	-----------------------	------------

Week# 4

Program Number: 4

TITLE:

 **WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT  
3.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING  
GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH  
TABLE**



≡ MUX2to1.v ×

≡ MUX2to1\_tb.v

≡ MUX2to1.v

```
1  module andgate(a,b,c);
2  input a,b;
3  output c;
4  assign c=a*b;
5  endmodule
6  module xorgate(a,b,c);
7  input a,b;
8  output c;
9  assign c=a^b;
10 endmodule
11 module orgate(a,b,c);
12 input a,b;
13 output c;
14 assign c=a|b;
15 endmodule
16 module fulladder(a,b,c,sm, co);
17 input a,b,c;
18 output sm,co;
19 wire W1, W2, W3;
20 xorgate F1 (a,b,W1);
21 andgate F2 (a,b,W2);
22 xorgate F3 (W1,c,sm);
23 andgate F4 (W1,c,W3);
24 orgate F5 (W2,W3,co);
25 endmodule
26 module circuit2 (a,b,c,d, sum, carry);
27 input a,b,c,d;
28 output sum, carry;
29 wire ws,wc;
30 fulladder f1 (a,b,c, ws, wo);
31 fulladder f2 (ws, wo,d, sum, carry);
32 endmodule
```

```

MUX2to1.v  MUX2to1_tb.v x
MUX2to1_tb.v
1  `define TESTVECS 4
2  module tb_fav;
3  reg a,b,c,d;
4  wire Sum;
5  wire Carry;
6  reg [3:0] test_vecs [0: (`TESTVECS)];
7  integer i;
8  initial begin
9      $dumpfile("fulladderv.vcd");
10     $dumpvars(0, tb_fav);
11 end
12 initial begin
13     test_vecs[0] = 4'b0000;
14     test_vecs[1] = 4'b0011;
15     test_vecs[2] = 4'b0100;
16     test_vecs[3] = 4'b0111;
17 end
18 circuit2 uut(a, b, c, d, Sum, Carry);
19 initial begin
20     for (i = 0; i < (`TESTVECS); i = i + 1) begin
21         #10 {a, b, c, d} = test_vecs[i];
22         $monitor("At time = %t, a = %b, b = %b, c = %b, d = %b, Sum = %b, Carry = %b",
23             $time, a, b, c, d, Sum, Carry);
24     end
25     #10 $finish;
26 end
27 endmodule

```

```

abhishekp@Abhisheks-MacBook-Air-3 verilog % iverilog -o dsn MUX2to1_tb.v MUX2to1.v

```

```

abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn

```

```

VCD info: dumpfile fulladderv.vcd opened for output.

```

```

At time =          10, a = 0, b = 0, c = 0, d = 0, Sum = 0, Carry = 0

```

```

At time =          20, a = 0, b = 0, c = 1, d = 1, Sum = 0, Carry = 1

```

```

At time =          30, a = 0, b = 1, c = 0, d = 0, Sum = 1, Carry = 0

```

```


At time =          40, a = 0, b = 1, c = 1, d = 1, Sum = 0, Carry = 1

```

```

MUX2to1_tb.v:31: $finish called at 50 (1s)

```

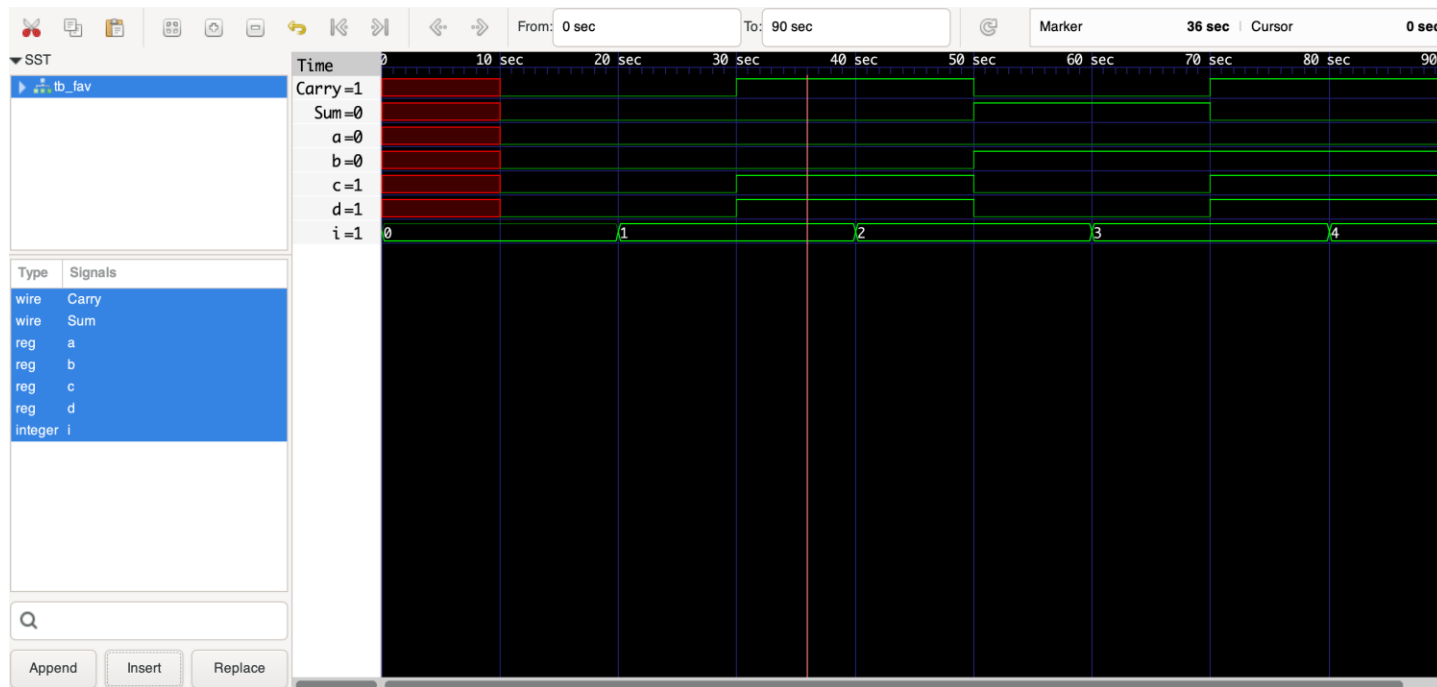

## Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Date: 09/09/2024

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------


Week# 4

Program Number: 5

TITLE:

WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT  
4.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING

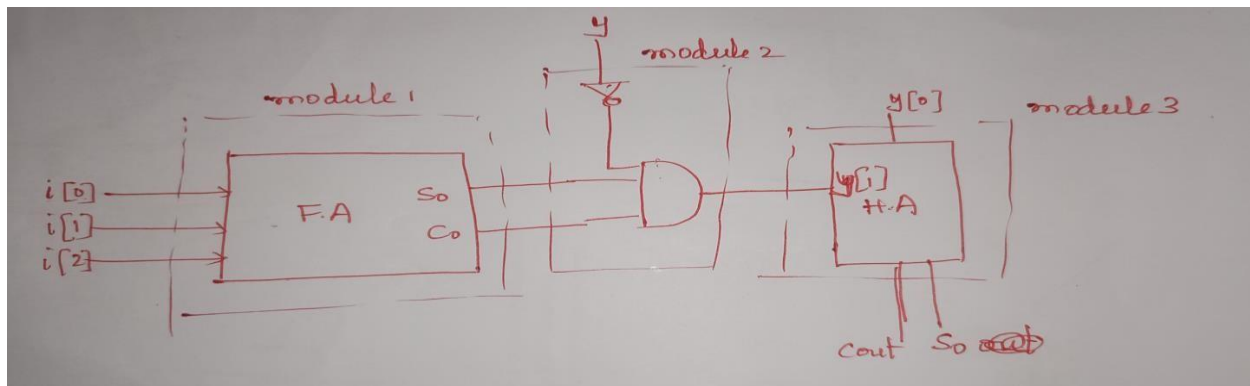**GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**



≡ MUX2to1.v ×

≡ MUX2to1\_tb.v

≡ MUX2to1.v

```
1  module andgate(a,b,c);
2  input a,b;
3  output c;
4  assign c = a * b;
5  endmodule
6  module and3gate(a,b,c,d);
7  input a,b,c;
8  output d;
9  assign d = a * b * c;
10 endmodule
11 module xorgate(a,b,c);
12 input a,b;
13 output c;
14 assign c = a ^ b;
15 endmodule
16 module orgate(a,b,c);
17 input a,b;
18 output c;
19 assign c = a | b;
20 endmodule
21 module notgate(
22     input a,
23     output y
24 );
25 assign y = !a;
26 endmodule
27 module fulladder (a, b, c, sm, co);
28 input a, b, c;
29 output sm, co;
30 wire W1, W2, W3;
31 xorgate F1(a, b, W1);
32 andgate F2(a, b, W2);
33 xorgate F3(W1, c, sm);
34 andgate F4(W1, c, W3);
35 orgate F5(W2, W3, co);
36 endmodule
37 module circuit2(a, b, c, d, e, sum, carry);
38 input a, b, c, d, e;
39 output sum, carry;
40 wire ws, wc, w1, W2;
41 fulladder f1(a, b, c, ws, wc);
42 notgate n1(d, w1);
43 and3gate a1(ws, wc, w1, W2);
44 fulladder f2(W2, e, 1'b0, sum, carry);
45 endmodule
```

```

MUX2to1.v  MUX2to1_tb.v x
MUX2to1_tb.v
1  `define TESTVECS 8
2  module tb_faw;
3  reg a,b,c,d,e;
4  wire Sum;
5  wire Carry;
6  reg [4:0] test_vecs [0: (`TESTVECS-1)];
7  integer i;
8  initial begin
9  $dumpfile("fulladderw.vcd");
10 $dumpvars(0, tb_faw);
11 end
12 initial begin
13 test_vecs[0]= 5'b00000;
14 test_vecs[1]= 5'b00100;
15 test_vecs[2] = 5'b01001;
16 test_vecs[3]= 5'b01101;
17 test_vecs[4]= 5'b10010;
18 test_vecs[5]= 5'b10110;
19 test_vecs[6]= 5'b11011;
20 test_vecs[7]= 5'b11111;
21 end
22
23 circuit2 uut (a,b,c,d,e, Sum, Carry);
24 initial begin
25 for (i = 0; i < (`TESTVECS); i = i + 1) begin
26 #10 {a,b,c,d,e} = test_vecs[i];
27 $monitor("At time=%t, i1[0] %b, i1[1]%b, i1[2]= %b, Y1 = %b, Y2 =%b Sum = %b, Carry %b",
28 $time, a, b, c, d, e, Sum, Carry);
29 end
30 #10 $finish;
31 end
32 endmodule


```

```

abhishekp@Abhisheks-MacBook-Air-3 verilog % iverilog -o dsn MUX2to1_tb.v MUX2to1.v
abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn
VCD info: dumpfile fulladderw.vcd opened for output.
At time=          10, i1[0] 0, i1[1]0, i1[2]= 0, Y1 = 0, Y2 =0 Sum = 0, Carry 0
At time=          20, i1[0] 0, i1[1]0, i1[2]= 1, Y1 = 0, Y2 =0 Sum = 0, Carry 0
At time=          30, i1[0] 0, i1[1]1, i1[2]= 0, Y1 = 0, Y2 =1 Sum = 1, Carry 0
At time=          40, i1[0] 0, i1[1]1, i1[2]= 1, Y1 = 0, Y2 =1 Sum = 1, Carry 0
At time=          50, i1[0] 1, i1[1]0, i1[2]= 0, Y1 = 1, Y2 =0 Sum = 0, Carry 0
At time=          60, i1[0] 1, i1[1]0, i1[2]= 1, Y1 = 1, Y2 =0 Sum = 0, Carry 0
At time=          70, i1[0] 1, i1[1]1, i1[2]= 0, Y1 = 1, Y2 =1 Sum = 1, Carry 0
At time=          80, i1[0] 1, i1[1]1, i1[2]= 1, Y1 = 1, Y2 =1 Sum = 1, Carry 0
MUX2to1_tb.v:30: $finish called at 90 (1s)

```



 

### Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

A handwritten signature in black ink on a light gray background. The signature is written in a cursive style and is underlined with a single horizontal stroke.

Signature:

Name: ABHISHEK P

SRN: PES2UG23AM002

Section: A

Date: 09/09/2024