

# Digital Design and Computer Organization Laboratory

3<sup>rd</sup> Semester, Academic Year 2024-25

Date:22/08/2024

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------

Week#\_\_2\_\_


Program Number :\_\_1\_\_

Title of the Program

SIMPLE\_CIRCUIT


Aim:

 WRITE A VERILOG PROGRAM TO MODEL THE GIVEN SIMPLE CIRCUIT.GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND WAVEFORM WITH THE RELEVANT TRUTH TABLE



```
1  module simple_circuit
2  (A,B,C,D,E);
3  output D,E;
4  input A,B,C;
5  wire w1;
6  and G1(w1,A,B);
7  not G2(E,C);
8  or G3(D,w1,E);
9  endmodule
10
```

```
abhishekp@Abhisheks-MacBook-Air-3 ~ % cd Downloads
abhishekp@Abhisheks-MacBook-Air-3 Downloads % cd verilog
abhishekp@Abhisheks-MacBook-Air-3 verilog % iverilog -o dsn and2.v and2_test.v
abhishekp@Abhisheks-MacBook-Air-3 verilog % vvp dsn
VCD info: dumpfile simple.vcd opened for output.
      0 A=0, B=0, C=0, D=1, E=1
     20 A=0, B=0, C=1, D=0, E=0
     40 A=0, B=1, C=0, D=1, E=1
     60 A=0, B=1, C=1, D=0, E=0
     80 A=1, B=0, C=0, D=1, E=1
    100 A=1, B=0, C=1, D=0, E=0
    120 A=1, B=1, C=0, D=1, E=1
    140 A=1, B=1, C=1, D=1, E=0
and2_test.v:23: $finish called at 200 (1s)
abhishekp@Abhisheks-MacBook-Air-3 verilog %
```

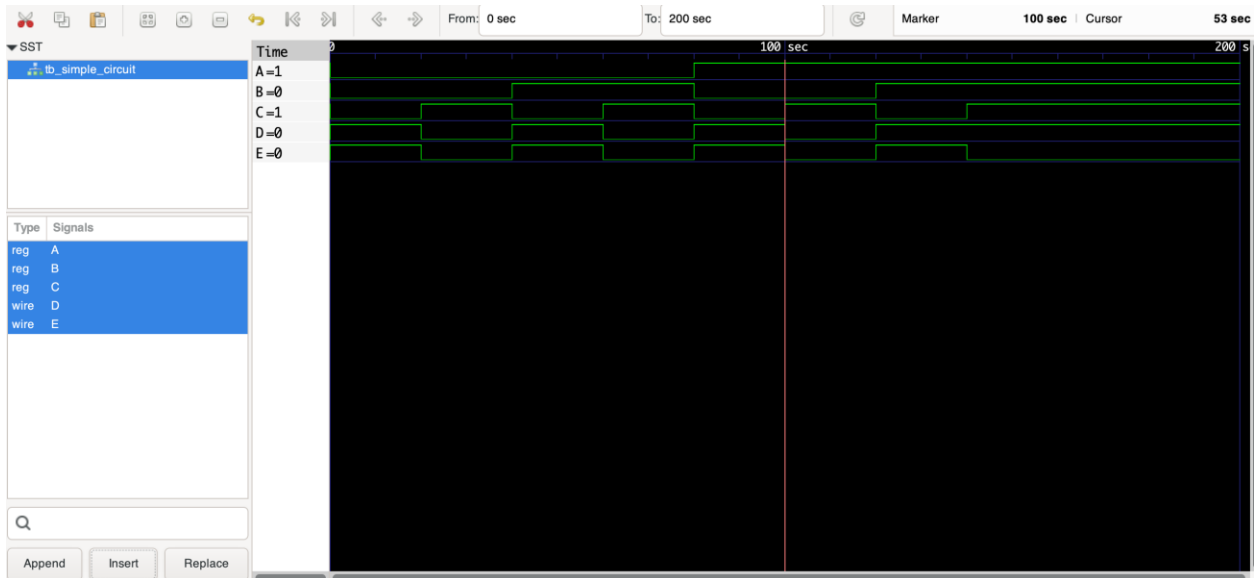

Date:22/08/2024

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------

Week#\_\_2\_\_


Program Number: \_\_2\_\_

Title of the Program


CIRCUIT1

Aim:

 **WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT1. GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND WAVEFORM WITH THE RELEVANT TRUTH TABLE**



```
and2.v and2_test.v x
and2_test.v
1  module tb_week2q1;
2  reg a,b,c;
3  wire d;
4  ckt M1(a,b,c,d);
5  initial
6  begin
7  #0
8  a=1'b0;b=1'b0;c=1'b0;
9  #20
10 a=1'b0;b=1'b0;c=1'b1;
11 #20
12 a=1'b0;b=1'b1;c=1'b0;
13 #20
14 a=1'b0;b=1'b1;c=1'b1;
15 #20
16 a=1'b1;b=1'b0;c=1'b0;
17 #20
18 a=1'b1;b=1'b0;c=1'b1;
19 #20
20 a=1'b1;b=1'b1;c=1'b0;
21 #20
22 a=1'b1;b=1'b1;c=1'b1;
23 end
24 initial
25 begin
26 $monitor($time,"a=%b,b=%b,c=%b,d=%b",a,b,c,d);
27 end
28 initial
29 begin
30 $dumpfile("test.vcd");
31 $dumpvars(0,tb_week2q1);
32 end
33 endmodule
```

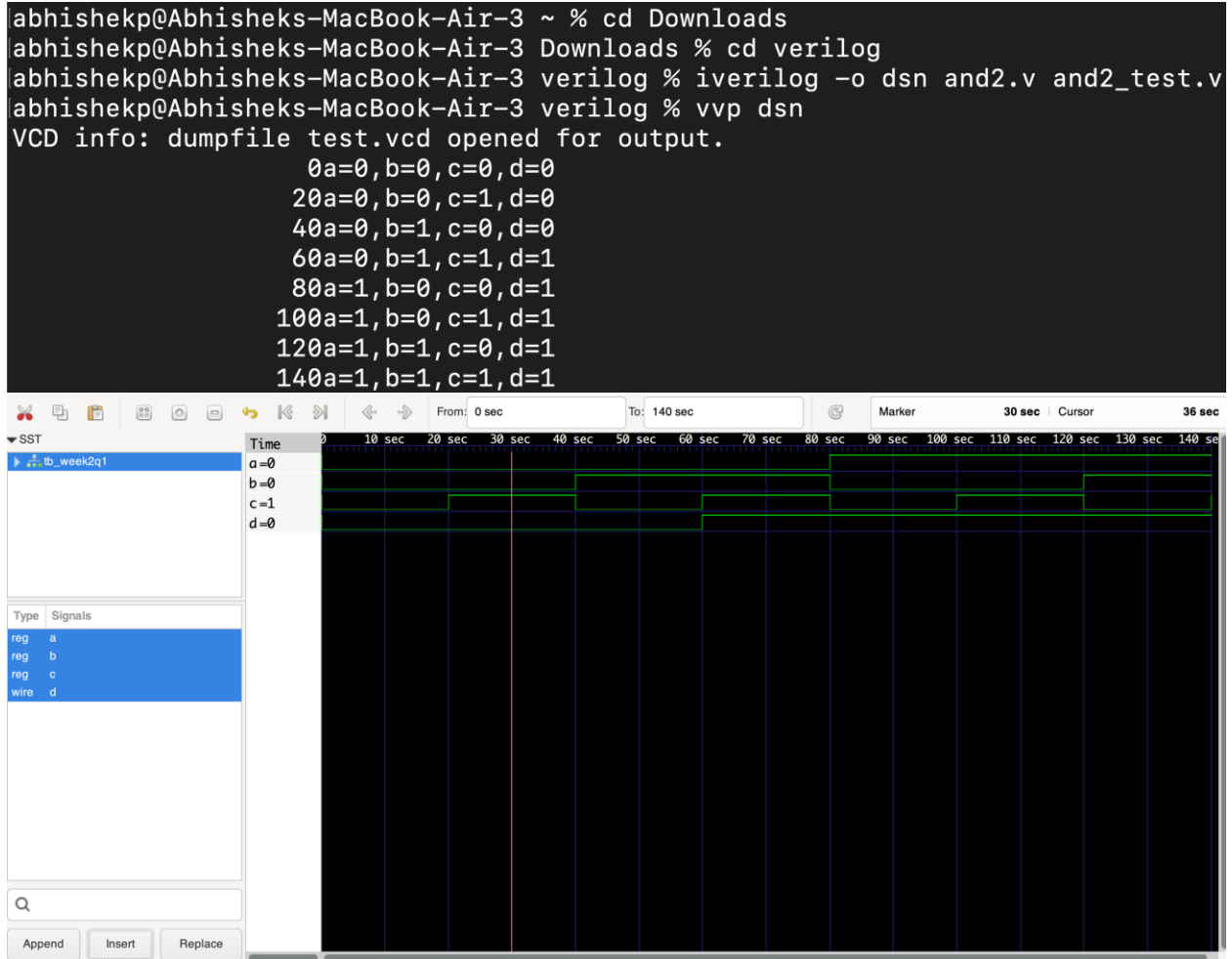

Date:22/08/2024

Name: ABHISHEK P	SRN: PES2UG23AM002	Section: A
------------------	--------------------	------------

Week#\_\_2\_\_\_\_\_

Program Number: \_\_\_\_3\_\_\_\_\_


Title of the Program

CIRCUIT2

Aim:

WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT2.  
GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION  
WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND  
WAVEFORM WITH THE RELEVANT TRUTH TABLE


CIRCUIT 2

 

```

module tb_week2q2;
  reg a2,b2,c2;
  wire z;
  ckt M1(a2,b2,c2,z);
  initial
  begin
    #0
    a2=1'b0;b2=1'b0;c2=1'b0;
    #20
    a2=1'b0;b2=1'b0;c2=1'b1;
    #20
    a2=1'b0;b2=1'b1;c2=1'b0;
    #20
    a2=1'b0;b2=1'b1;c2=1'b1;|
    #20
    a2=1'b1;b2=1'b0;c2=1'b0;
    #20
    a2=1'b1;b2=1'b0;c2=1'b1;
    #20
    a2=1'b1;b2=1'b1;c2=1'b0;
    #20
    a2=1'b1;b2=1'b1;c2=1'b1;
  end
  initial
  begin
    $monitor($time,"a2=%b,b2=%b,c2=%b,z=%b",a2,b2,c2,z);
  end
  initial
  begin
    $dumpfile("test.vcd");
    $dumpvars(0,tb_week2q2);
  end
endmodule


```

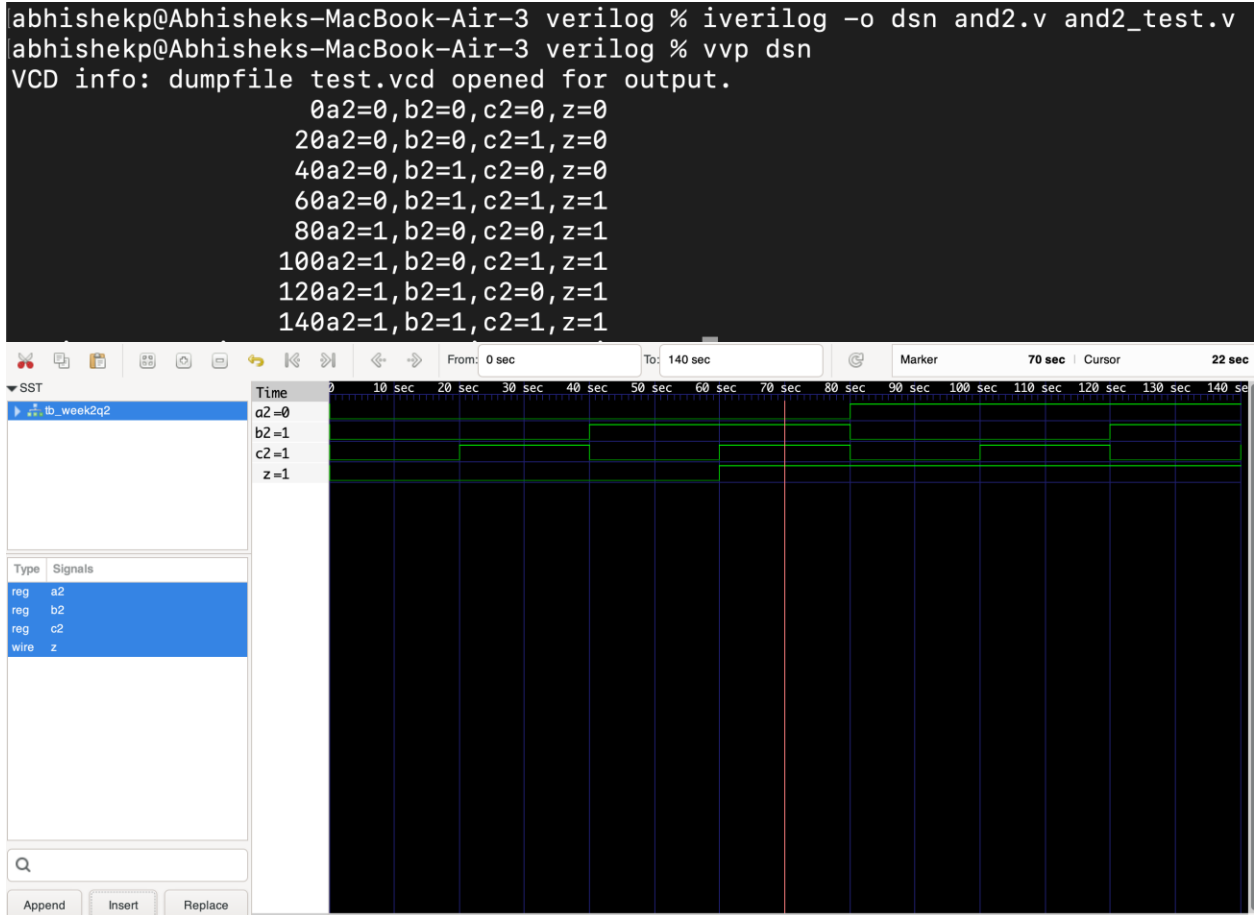
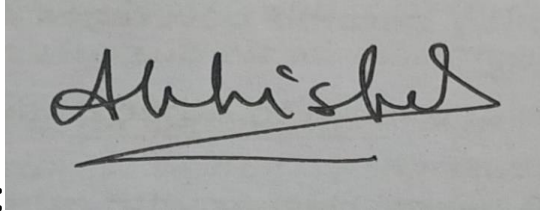
## Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.



A rectangular box containing a handwritten signature in black ink. The signature appears to be 'Abhishek' written in a cursive style, with a horizontal line underneath the name.

Signature:

Name: ABHISHEK P

SRN: PES2UG23AM002

Section: A

Date: 22/08/2024